

B.Tech-2nd(Sec-D, E, F, G, H, I & J)

Basic Electronics

Full Marks : 50

Time : $2\frac{1}{2}$ hours

Answer **all** questions.

The figures in the right-hand margin indicate marks

Symbols carry usual meaning

1. Answer *all* questions : 2 × 5

- (a) How does BJT acts as a switch ?
- (b) List the advantages of FET over BJT.
- (c) Explain virtual ground concept in case of ideal OPAMP.
- (d) Convert $(ABC)_{16}$ into decimal and octal.
- (e) Draw detailed diagram of CRT.

(Turn Over)

(2)

2. (a) A centre tap rectifier uses a Si diode of resistance 25Ω . The secondary voltage from centre to each end of secondary is 120v (rms). If the load resistance of $1 K\Omega$ is connected across this rectifier, calculate I_{dc} and I_{rms} . 4

(b) Explain common base characteristic curves of NPN transistor. 4

Or


(a) Explain step by step procedure of monolithic IC fabricating for NPN transistor. 4

(b) Explain why CE configuration preferred as an amplifier. 4

3. (a) Explain the working of Enhancement type n-channel MOSFET. 4

(3)

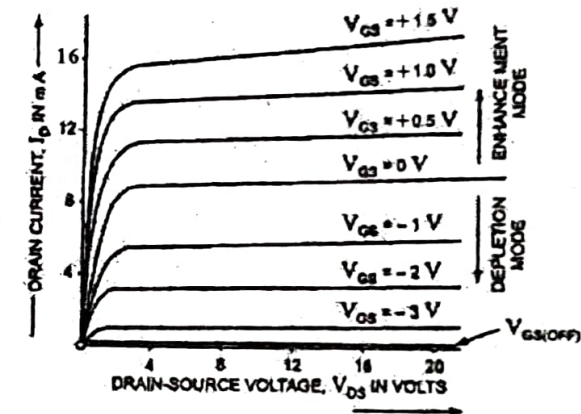(b) From the given drain characteristic identify the device and draw its transfer characteristics using graphical method. 4




Or

(a) Explain the construction and working of P-channel JFET. 4

(b) (i) A JFET has a drain current of 5 mA. If $I_{DSS} = 10 \text{ mA}$ and $V_{GS(off)} = -6 \text{ V}$, Find the value of (a) V_{GS} and (b) V_P .

(4)

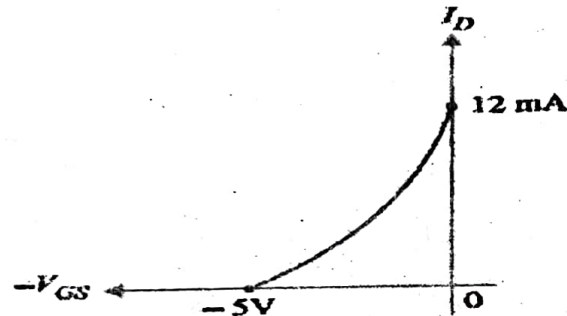
- (ii) From the transfer characteristic of JFET shown in given figure, write the equation for drain current. 4



4. (a) Explain modes of operation of OPAMP. 4
(b) Compare negative and positive feedback along with their block diagrams. 4

Or

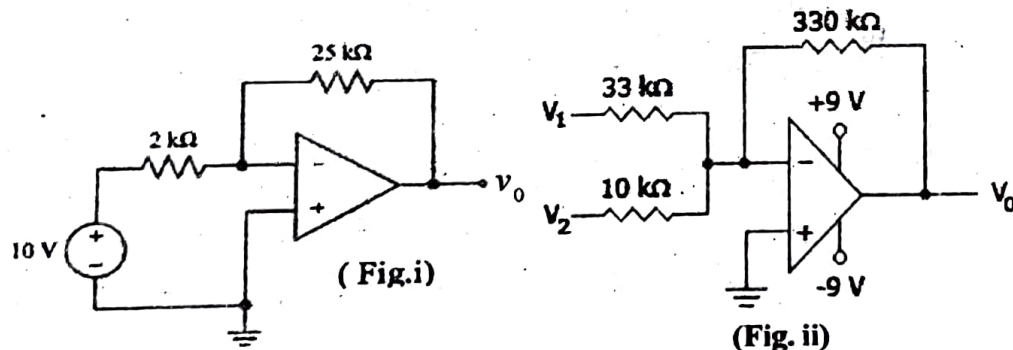- (a) Calculate v_o in Fig. i and V_o in Fig. ii. 4



(5)

- (b) Prove that input impedance increases and output impedance decreases in voltage series feedback. 4

5. (a) State the Absorption law and De-Morgans theorem. Apply the De-Morgans theorem to following expression

$$\overline{AB + \overline{CD} + BD}$$

- (b) Using Boolean algebra, simplify the following 4

(i) $AB + A(B + C) + B(B + C)$

(ii) $(\overline{AB}(C + BD)\overline{AB})C$

Or

- (a) Write the truth table of $F = \overline{A} + BC + CD$ and draw the logic diagram using basic gates. 4

(b) Implement the following logic functions 4

(i) $X = \bar{A} + BC$ using NAND gates only

(ii) $Y = \bar{A}B + C$ using NOR gates only.

6. (a) Explain amplitude modulation in details. 4

(b) List different applications of CRO. 4

Or

(a) Explain the block diagram of DSO. 4

(b) Compare AM and FM. 4
